

GATE 2023 Computer Science and Information Technology (CS)

November 10, 2023

1. The output of a 2-input multiplexer is connected back to one of its inputs as shown in the figure.

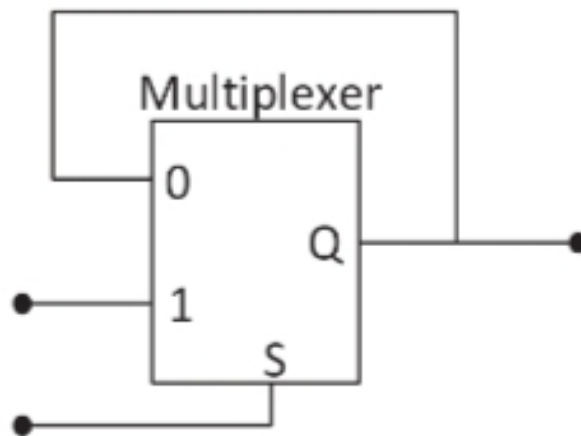


Figure 1: circuit

2. Match the functional equivalence of the circuit to one of the following options.
 - (a) D Flip-flop
 - (b) D Latch
 - (c) Half-adder
 - (d) Demultiplexer