

back to one of its inputs as shown in the figure.

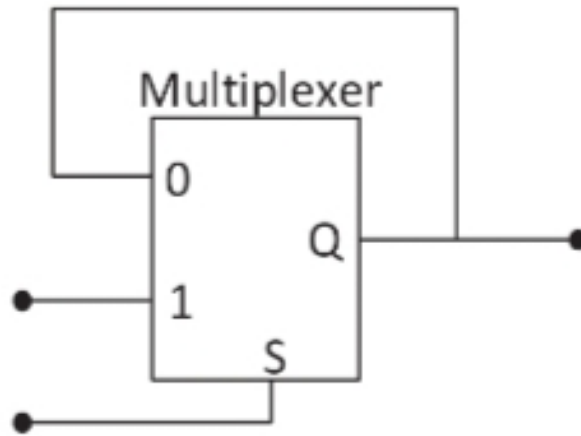


Figure 1: circuit

1. Match the functional equivalence of the circuit to one of the following options.
  - (a) D Flip-flop
  - (b) D Latch
  - (c) Half-adder
  - (d) Demultiplexer